

EC10508 / EC-1058 Basic Electronics

I B.E./B.TECH EXAMINATION


Time 3 hrs.

Max Marks:70

Min Marks: 22

NOTE: Attempt all the questions. All carry equal marks. All abbreviations carry their usual meanings.

TOTAL QUESTIONS - 05

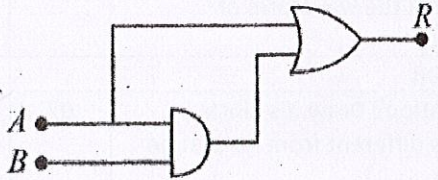Q. No		Question	Marks	CO	BL	PI
1	a	Explain the formation of Depletion layer in a PN junction.	02	1	1	1.4.1
	b	Sketch the V – I characteristics of a P N junction Diode.	02	1	1	1.4.1
	c	How does Zener Diode regulate the voltage? Explain.	03	1	2	1.4.1
	d	What is the difference between Half wave and Full wave rectifier? Draw the circuit diagram of Bridge Rectifier with labelled input and output waveform.	07	1	2	1.4.1
		OR				
	e	Explain the working of NPN CE transistor amplifier. Also draw its input and output characteristics and indicate different regions of importance.	07	1	2	1.4.1
2	a	Explain the working of Depletion type MOSFET.	02	2	1	1.4.1
	b	Explain the Virtual Ground Concept in an Operational Amplifier.	02	2	2	1.4.1
	c	Bringout a pointwise comparison between JFET and MOSFET.	03	2	2	1.4.2
	d	Explain with the help of neat diagrams, the structure of an N channel FET and it's volt-ampere characteristics.	07	2	3	1.4.1
		OR				
	e	What are characteristics of an OP-Amp? Also draw circuit diagram of OP-Amp as an Adder and Integrator.	07	2	3	1.4.1
3	a	A combinational circuit of logic gate is shown in circuit below, if A is at 3V and B is at 0V, then what will be potential at R ? 	02	3	2	1.4.1
	b	State true or false for statements given below	02	3	1	1.4.1

		<p>i. OR gate can be implemented using three NOR gates.</p> <p>ii. NAND gate give output 1, when any input is 1.</p>				
	c	<p>Solve the following</p> <p>i. Convert $(478.39)_{10}$ into octal</p> <p>ii. $(11000101101)_{\text{Gray}}$ into Binary</p> <p>iii. Prove $(X+Y)(X+Z) = X+YZ$</p>	03	3	2	1.4.1
	d	<p>What are combinational circuits? Describe, how a 3-bit adder can be implemented along with its circuit diagram and corresponding equations.</p>	07	3	3	1.4.1
		OR				
	e	<p>Simplify the expressions given below using K-map & implement the circuit diagrams for simplified expressions.</p> <p>i. $F = A'B'C' + A'B'C + A'BC + ABC + ABC'$</p> <p>ii. $F(A, B, C) = \sum m(0,1,5,6,7)$</p>	07	3	2	1.4.2
4	a	<p>What is Flip Flop? Write its applications?</p>	02	4	1	1.4.1
	b	<p>State the "Invalid state" of RS flip-flop. Give reason, why is it generated?</p>	02	4	2	1.4.1
	c	<p>Draw the circuit diagram of 4-bit binary weighted resistor DAC for input data 1010 and find output voltage?</p>	03	4	2	1.4.1
	d	<p>Realize J-K flip-flop with circuit diagram & characteristics table. Deduce its characteristics equation. Illustrate working in detail.</p>	07	4	3	1.4.1
		OR				
	e	<p>What is the significance of ADC & DAC? Using appropriate diagram, explain any one type of analog to digital converter in detail.</p>	07	4	3	1.4.1
5	a	<p>Define Modulation. Why is it needed?</p>	02	5	1	1.4.1
	b	<p>How DSO is advantageous over CRO?</p>	02	5	1	1.4.1
	c	<p>Differentiate between Sensors and Transducers.</p>	03	5	2	1.4.1
	d	<p>Draw and explain block diagram of Communication System. Also sketch and label the waveform of Amplitude modulated wave.</p>	07	5	3	1.4.1
		OR				
	e	<p>What is Pulse Code Modulation? Draw its block diagram and show how it is different from Amplitude and Frequency Modulation.</p>	07	5	3	1.4.3